

# ECE451Lab2

Huanjia Liu (ID:831993149)

Sep 25, 2020

# Contents

<b>1</b>	<b>Objective</b>	<b>3</b>
<b>2</b>	<b>Introduction</b>	<b>3</b>
<b>3</b>	<b>Procedure</b>	<b>3</b>
3.1	Verilog Code . . . . .	3
3.1.1	Declare part . . . . .	3
3.1.2	Function part . . . . .	4
3.1.3	Display part . . . . .	5
3.2	Simulation . . . . .	9
3.3	FPGA running . . . . .	10
<b>4</b>	<b>Question</b>	<b>11</b>
4.1	Discuss the advantages of a Hardware Descriptive Language (HDL). . . . .	11
<b>5</b>	<b>Conclusion</b>	<b>11</b>

# 1 Objective

During this lab, we are asked to learn the basic logic synthesis steps by synthesizing a 3-bit signed Arithmetic Logic Unit (ALU) using Verilog. on PC with a Linux OS for Quartus and ModelSim, FPGA Board.

## 2 Introduction

Verilog, standardized as IEEE 1364, is a hardware description language (HDL) used to model electronic systems. It is most commonly used in the design and verification of digital circuits at the register-transfer level of abstraction.

In Lab2, we should design a 3 bits ALU again like Lab1, but this time, we use more convenient way: Verilog.

There are 4 kinds of input: fun\_sel0 and fun\_sel1: Selects one of the four functions. ain[2:0] and bin[2:0]: Inputs for the two 3-bit numbers or one 3-bit number. Also there is one output: out[2:0]: The three-bit number that is the result of the ALU operation. Also a little different with Lab1, we need 2 digits 7-segment display control output to show the final result on 7-segment display.

As for our 3 bits ALU, four functions are combined: three-bit addition, subtraction, XOR (bitwise between A and B), and 3-bit shift-left (on A; shift in zero at the least significant bit).

## 3 Procedure

### 3.1 Verilog Code

We can divide Verilog Code to three part. Declare part, function part, segment display part.

#### 3.1.1 Declare part

Here we declare three input and three output. Sel means select, which is used to select mode of ALU, the LED\_out and LED\_outs are the variable to control first and second 7-segment.

---

```
module lab2(A, B, Sel, V_out, LED_out, LED_outs);
```

```

input[2:0] A,B;

input[1:0] Sel;

//output reg C_out;

output reg [3:0] V_out;

output reg [6:0] LED_out;

output reg [6:0] LED_outs;

```

---

### 3.1.2 Function part

Here we use Verilog code to achieve four function (addition, subtraction, XOR, and 3-bit shift-left) in different Sel mode. We are asked to display two 7-segment, thus, 4 bit V\_out is required.

---

```

reg [3:0] temp;

always @ (A, B, Sel)
begin
    case(Sel)
        2'b00:
            begin
                V_out = {1'b0, A} + {1'b0, B};
                //C_out = temp[3];
                //V_out = temp[2:0];
            end

        2'b01:
            begin
                V_out = {1'b0, A} - {1'b0, B};
                //C_out = temp [3];
            end
    endcase
end

```

```

        //V_out = temp[2:0];

    end

    2'b10: V_out = {1'b0,A~B};

    2'b11:

    begin

        V_out = {1'b0, A} << 1;

        //C_out = temp[3];

        //V_out = temp[2:0];

    end

endcase

end

```

---

### 3.1.3 Display part

Now, we can use the variable `V_out` come from function part to display number on two 7-segment. 0 means led light on, while 1 means led light off.

---

```

always @(*)

begin

    case(V_out)

        4'b0000:

        begin

            LED_out = 7'b1000000; // "0"

            LED_outs = 7'b1000000;

        end

        4'b0001:

        begin

            LED_out = 7'b1111001; // "1"

            LED_outs = 7'b1000000;

        end

    end

```

```
4'b0010:

begin

LED_out = 7'b0100100; // "2"

LED_outs = 7'b1000000;

end
```

```
4'b0011:

begin

LED_out = 7'b0110000; // "3"

LED_outs = 7'b1000000;

end
```

```
4'b0100:

begin

LED_out = 7'b0011001; // "4"

LED_outs = 7'b1000000;

end
```

```
4'b0101:

begin

LED_out = 7'b0010010; // "5"

LED_outs = 7'b1000000;

end
```

```
4'b0110:

begin

LED_out = 7'b0000010; // "6"

LED_outs = 7'b1000000;
```

```
end
```

```
4'b0111:
```

```
begin
```

```
LED_out = 7'b1111000; // "7"
```

```
LED_outs = 7'b1000000;
```

```
end
```

```
4'b1000:
```

```
begin
```

```
LED_out = 7'b0000000; // "8"
```

```
LED_outs = 7'b1000000;
```

```
end
```

```
4'b1001:
```

```
begin
```

```
LED_out = 7'b0010000; // "9"
```

```
LED_outs = 7'b1000000;
```

```
end
```

```
4'b1010:
```

```
begin
```

```
LED_out = 7'b1000000; // "10"
```

```
LED_outs = 7'b1111001;
```

```
end
```

```
4'b1011:
```

```
begin
```

```
LED_out = 7'b1111001; // "11"
```

```

    LED_outs = 7'b1111001;

end

4'b1100:

begin

    LED_out = 7'b0100100; // "12"

    LED_outs = 7'b1111001;

end

4'b1101:

begin

    LED_out = 7'b0110000; // "13"

    LED_outs = 7'b1111001;

end

4'b1110:

begin

    LED_out = 7'b0011001; // "14"

    LED_outs = 7'b1111001;

end

4'b1111:

begin

    LED_out = 7'b0010010; // "15"

    LED_outs = 7'b1111001;

end

```



```

default: LED_out = 7'b1000000; // "0"

endcase

end

```

---

## 3.2 Simulation

Before compiling and downloading code into FPGA board, I create a VWF file in the Quartus to simulate my design.

At first, I simulate function part with 7-segment display. Here are four function test result.

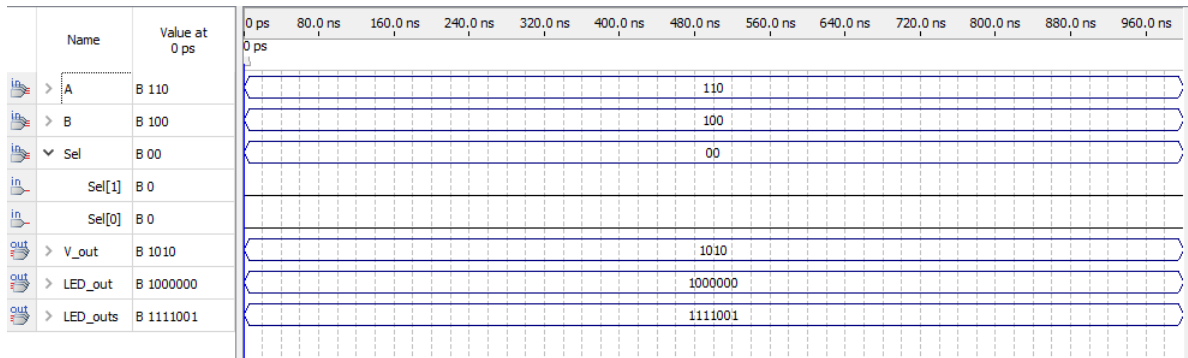


Figure 1: 6(110) plus 4(100)

 


Figure 2: 6(110) plus 4(100)

 


Figure 3: 6(110) xor 4(100)

 


Figure 4: 6(110) left shift 1 bit

### 3.3 FPGA running

As simulation works pretty well, I edit pin planner and download the code into FPGA, and show the result to TA.

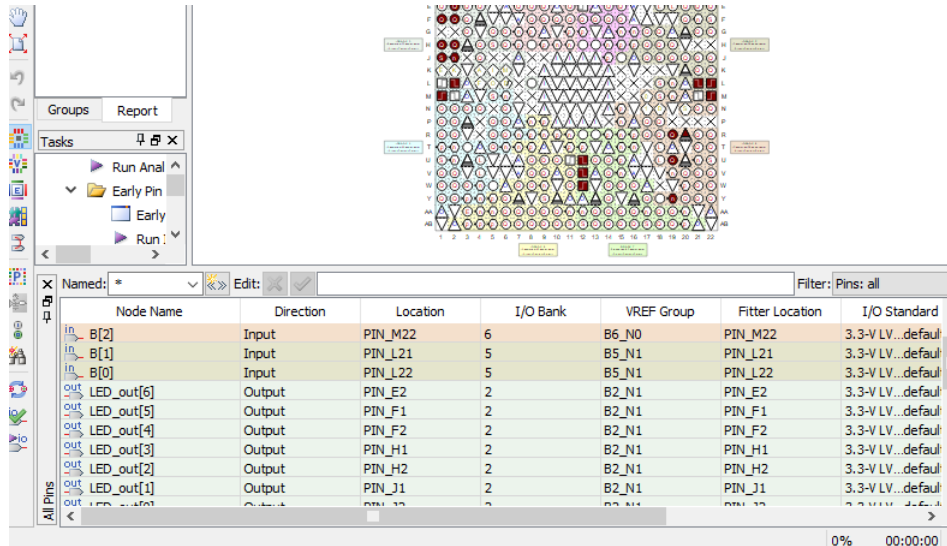


Figure 5: Pin Planner

## 4 Question

### 4.1 Discuss the advantages of a Hardware Descriptive Language (HDL).

Process-independence and significantly shorter design cycles. This allows the engineer to design the actual circuit in the functional design, logic verification stage without having to consider too much about the gate level and the specific details of the process implementation, and only need to use the requirements of the chip in the system design and impose different constraints.

## 5 Conclusion

Now we can get the conclusion, I finish this lab successfully, and achieve all the objective.