

# ECE451Lab4

Huanjia Liu (ID:831993149)

Oct 30, 2020

# Contents

|          |  |           |
|----------|--|-----------|
| <b>1</b> | <b>Objective</b>   | <b>3</b>  |
| <b>2</b> | <b>Introduction</b>  | <b>3</b>  |
| 2.1      | Candence Part . . . . .  | 3         |
| 2.2      | Verilog Part . . . . .   | 3         |
| <b>3</b> | <b>Procedure and analysis</b>                                      | <b>4</b>  |
| 3.1      | Candence Part . . . . .  | 4         |
| 3.2      | Verilog Part . . . . .   | 6         |
| <b>4</b> | <b>Questions</b>   | <b>10</b> |
| 4.1      | Discuss the concept and advantages of hierarchical design. . . . . | 10        |
| 4.2      | How was hierarchical design utilized in this lab? . . . . .        | 11        |
| <b>5</b> | <b>Conclusion</b>  | <b>11</b> |
| <b>6</b> | <b>Appendix</b>  | <b>11</b> |

# 1 Objective

During this lab, we are asked to design a ROM circuit in the Candence to store some message and write a Verilog program to achieve displaying frame on 8\*8 LED matrix. And here are the general objective we need to realize.

- 1 Use hierarchical design to create complex circuits
- 2 Understand the design and function of a ROM and Decoder
- 3 Blinkenlights!

## 2 Introduction

### 2.1 Candence Part

In Candence part, we are asked to Use a 7xN ROM to write an English word or phrase at least 5 ASCII characters long to the output. The input is a char select number, in range:  $[\log_2 N, 0]$ . And the output is the ASCII format characters which is stored in ROM.

### 2.2 Verilog Part

In Verilog part, we are asked to use a ROM to display a sequence of frames to an 8x8 LED matrix. We must use at least 4 different frames. The frame rate should be 0.25 Hz at the slowest. (4 seconds per frame). We may make the frame rate as fast as necessary, so long as it is apparent that you are using multiple frames. As a guideline, 8-15 Hz should be sufficient for a simple animation. There are three input: clock50MHZ, run, reset. And two output 8 bits row data and 8 bits column data. Finally the output pins will connect to LED matrix to realize displaying.

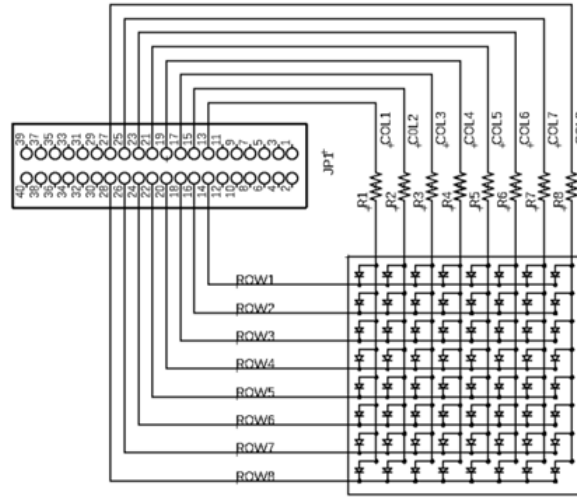


Figure 1: LED matrix circuit

### 3 Procedure and analysis

#### 3.1 Candence Part

In order to implement ROM, decoder is require, here is my circuit of 3:8 decoder.

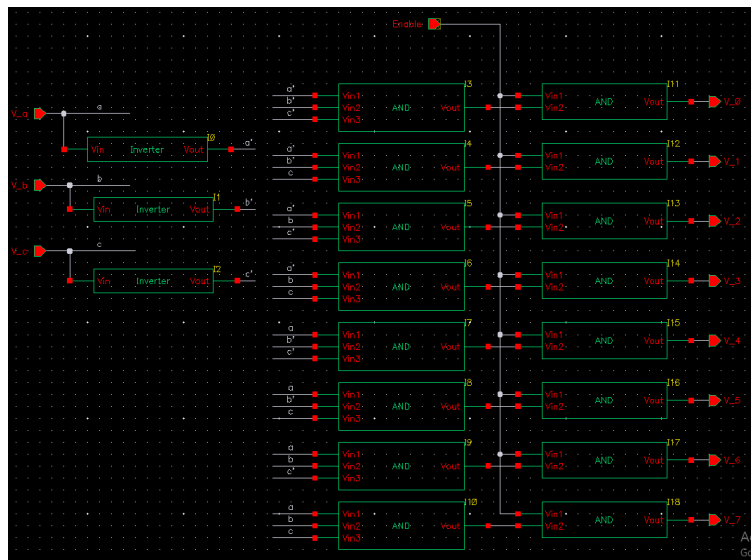


Figure 2: LED matrix circuit

Also here is my wave of decoder from to confirm my circuit works well.

 


Figure 3: Waveform of 3:8 decoder

Then adding the decoder to ROM circuit, here is the circuit (the green block is 3-8 decoder) and the waveform after simulating. The words I store in ROM is "GO RAMS ".

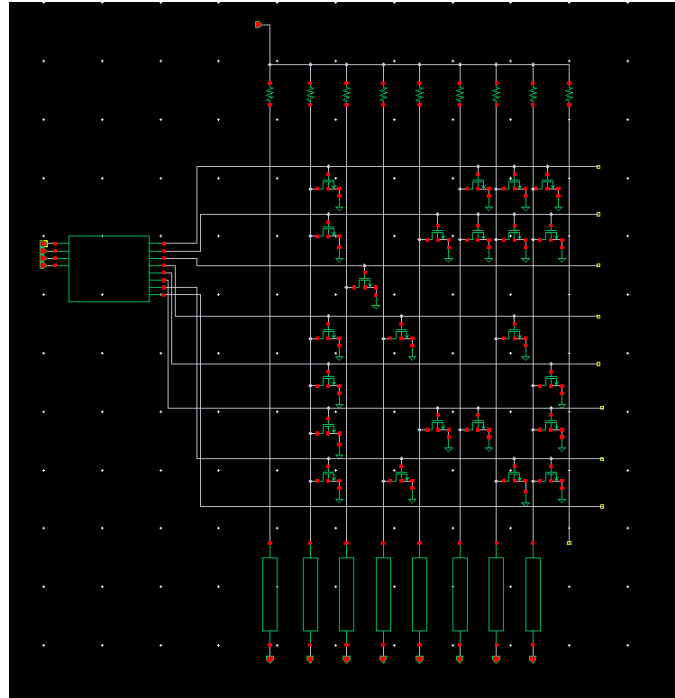


Figure 4: ROM circuit

 


Figure 5: Final display

### 3.2 Verilog Part

In Verilog part, the most important part is clock divider module, here I use 50MHZ crystal oscillator clock generate from my FPGA DE1 board.

---

```

reg [12:0] row_counter;

reg clk_counter;

always @(posedge clk)
begin
    if(row_counter ==0 )
    begin
        clk_counter <= ~clk_counter;

    end

    row_counter <= row_counter +1;
end
end

```

---

Variable **row\_counter** can control the clock time length, and variable **clk\_counter** is the new clock signal

be created whose period is depend on **row\_counter**

Then is the LED display part, **frame** control the picture which will be displayed on LED matrix, we are asked to display 4 pictures, thus, I use 2 bit to declare **frame**. Varibale **z** control the delay time between four frames, and variable **i** control the update rate LED matirx. By the way, I add run pin here: when run pin is on, **z** will keep count, however, if run pin is off, **z** will keep same which means variable **frame** which is controlled by the **z** will keep same, so that the frame be displayed will keep same.

---

```
reg [3:0] i = 3'b000;
reg [12:0] z;
reg [1:0] frame = 2'b00;
always @(posedge clk_counter)
begin
    case(frame)
        2'b01:
            begin
                case(i)
                    \\ROM part, I will explain it later.
                endcase;
            end
        2'b10:
            begin
                case(i)
                    \\ROM part, I will explain it later.
                endcase;
            end
        2'b11:
            begin
                case(i)
```

```

        \\ROM part, I will explain it later.

    endcase;

end

2'b00:

begin

    case(i)

        \\ROM part, I will explain it later.

    endcase;

end

endcase

i = i+3'b001;

if(run)

begin

    z <= z + 1;

end

if(z == 0)

begin

    frame <= frame+1;

end

if(reset)

begin

    frame <= 2'b01;

end

end

```

---

The code below is LED matrix display, each case only display one column, but if the update rate is quick enough, all the columns will combine together because of visual residue. (hline control which column will be



displayed, and vline control the picture data).

---

```
case(i)

    3'b000:

        begin

            hline = 8'b01111111;

            vline = 8'b10000101;

        end

    3'b001:

        begin

            hline = 8'b10111111;

            vline = 8'b10000101;

        end

    3'b010:

        begin

            hline = 8'b11011111;

            vline = 8'b10000101;

        end

    3'b011:

        begin

            hline = 8'b11101111;

            vline = 8'b10000101;

        end

    3'b100:

        begin

            hline = 8'b11110111;
```

```

        vline = 8'b10000101;
    end

    3'b101:
    begin
        hline = 8'b11111011;
        vline = 8'b10000101;
    end

    3'b110:
    begin
        hline = 8'b11111101;
        vline = 8'b10000101;

    end

    3'b111:
    begin
        hline = 8'b11111111;
        vline = 8'b00000000;

    end
endcase

```

---

I will attach complete code in appendix, reader can get it from there.

## 4 Questions

### 4.1 Discuss the concept and advantages of hierarchical design.

Hierarchy in circuit design refers to the creation of higher level cells based on lower level cells. For example, if you create a cell that is composed of inverters and nand gates, you can instantiate (add) your previously designed inverter and nand cells rather than recreating them in the higher level cell.

## 4.2 How was hierarchical design utilized in this lab?

For example, in Candence part, we use the and, or, not gate which have already be designed in past lab, and that's is so convenient, that we don't need to consider the transistor level anymore, just use it. Also, the 3 to 8 decoder, we design it before we create our final circuit, so we can just use the block, and don't need to consider the circuit layout.

## 5 Conclusion

Now we can get the conclusion, I finish this lab successfully, and achieve all the objective. I have learned two important knowledge during this lab. First, there are some crystal oscillators in each board, we can use them to generate any delay time length we want. Second, do not connect the component to the voltage source without measuring the voltage level, since I burned my 8\*8 LED matrix because connect to FPGA board without resistor.

## 6 Appendix

---

```
module Lab4(run,reset,clk,vline,hline);

input wire clk;
input run;
input reset;
//input wire run;
//input wire reset;

output reg [7:0] vline;
output reg [7:0] hline;

reg [12:0] row_counter;
reg clk_counter;
```

```

reg [3:0] i = 3'b000;

reg [12:0] z;

reg [1:0] frame = 2'b00;


always @(posedge clk)

begin

    if(row_counter ==0 )

    begin

        clk_counter <= ~clk_counter;

    end

    row_counter <= row_counter +1;

end


always @(posedge clk_counter)

begin


    case(frame)

    2'b01:

    begin

        case(i)

        3'b000:

        begin

            hline = 8'b01111111;

            vline = 8'b10000101;


```

end

3'b001:

begin

hline = 8'b10111111;

vline = 8'b10000101;

end

3'b010:

begin

hline = 8'b11011111;

vline = 8'b10000101;

end

3'b011:

begin

hline = 8'b11101111;

vline = 8'b10000101;

end

3'b100:

begin

hline = 8'b11110111;

vline = 8'b10000101;

end

3'b101:

begin

hline = 8'b11111011;

vline = 8'b10000101;

```

end

3'b110:

begin

    hline = 8'b11111101;

    vline = 8'b10000101;

end

3'b111:

begin

    hline = 8'b11111111;

    vline = 8'b00000000;

end

endcase

end

2'b10:

begin

    case(i)

    3'b000:

    begin

        hline = 8'b01111111;

        vline = 8'b11110101;

    end

    3'b001:

    begin

```

```

        hline = 8'b10111111;

        vline = 8'b10000101;


end

3'b010:

begin

        hline = 8'b11011111;

        vline = 8'b10000101;

end

3'b011:

begin

        hline = 8'b11101111;

        vline = 8'b11110101;


end

3'b100:

begin

        hline = 8'b11110111;

        vline = 8'b00010101;

end

3'b101:

begin

        hline = 8'b11111011;

        vline = 8'b00010101;


end

3'b110:

begin

        hline = 8'b11111101;

```

```

        vline = 8'b11110101;

    end

    3'b111:

    begin

        hline = 8'b11111111;

        vline = 8'b00000000;

    end

    endcase

end

2'b11:

begin

    case(i)

    3'b000:

    begin

        hline = 8'b01111111;

        vline = 8'b11110101;

    end

    3'b001:

    begin

        hline = 8'b10111111;

        vline = 8'b10000101;

    end

    3'b010:

```



```

begin

    hline = 8'b11011111;

    vline = 8'b10000101;

end

3'b011:

begin

    hline = 8'b11101111;

    vline = 8'b11110101;

end

3'b100:

begin

    hline = 8'b11110111;

    vline = 8'b10000101;

end

3'b101:

begin

    hline = 8'b11111011;

    vline = 8'b10000101;

end

3'b110:

begin

    hline = 8'b11111101;

    vline = 8'b11110101;

end

3'b111:

begin

```

```

        hline = 8'b11111111;

        vline = 8'b10000101;

    end

    endcase

end

2'b00:

begin

    case(i)

        3'b000:

            begin

                hline = 8'b01111111;

                vline = 8'b10010101;

            end

        3'b001:

            begin

                hline = 8'b10111111;

                vline = 8'b10010101;

            end

        3'b010:

            begin

                hline = 8'b11011111;

                vline = 8'b10010101;

            end

        3'b011:

```

```

begin

    hline = 8'b11101111;

    vline = 8'b11110101;


end

3'b100:

begin

    hline = 8'b11110111;

    vline = 8'b10000101;

end

3'b101:

begin

    hline = 8'b11111011;

    vline = 8'b10000101;


end

3'b110:

begin

    hline = 8'b11111101;

    vline = 8'b10000101;


end

3'b111:

begin

    hline = 8'b11111111;

    vline = 8'b00000000;


end

endcase

```

```
end

endcase

i = i+3'b001;

if(run)

begin

    z <= z + 1;

end

if(z == 0)

begin

    frame <= frame+1;

end

if(reset)

begin

    frame <= 2'b01;

end

end

endmodule
```

---